

# **S2R72A54**

## **Application Note**

## NOTICE

---

No part of this material may be reproduced or duplicated in any form or by any means without the written permission of Seiko Epson. Seiko Epson reserves the right to make changes to this material without notice. Seiko Epson does not assume any liability of any kind arising out of any inaccuracies contained in this material or due to its application or use in any product or circuit and, further, there is no representation that this material is applicable to products requiring high level reliability, such as, medical products. Moreover, no license to any intellectual property rights is granted by implication or otherwise, and there is no representation or warranty that anything made in accordance with this material will be free from any patent or copyright infringement of a third party. When exporting the products or technology described in this material, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You are requested not to use, to resell, to export and/or to otherwise dispose of the products (and any technical information furnished, if any) for the development and/or manufacture of weapon of mass destruction or for other military purposes.

All brands or product names mentioned herein are trademarks and/or registered trademarks of their respective companies.

## Table of Contents

<b>1. Overview</b> .....	<b>1</b>
<b>2. Power Mode Description</b> .....	<b>2</b>
2.1 VBUS power supply mode settings.....	2
2.2 Treatment of downstream port not used .....	6
<b>3. PCB Design Guide</b> .....	<b>7</b>
3.1 Power supply configuration .....	7
3.2 Power supply and resetting .....	8
3.3 DP/DM signal line .....	11
3.3.1 Circuit board wiring .....	11
3.3.2 Additional components .....	11
3.3.3 Terminations .....	13
3.4 U0_VBUS pin protection circuit (upstream port side).....	14
3.5 VBUS supply circuit (downstream port side).....	15
3.6 Oscillator circuit .....	18
3.7 Other precautions.....	19
<b>4. Appendix</b> .....	<b>20</b>
4.1 DP/DM circuit board wiring examples.....	20
4.2 Upstream port connection example .....	21
4.3 Downstream port overcurrent detection example.....	23
4.4 Device malfunction detection and recovery .....	25
<b>Revision History</b> .....	<b>26</b>

### 1. Overview

This document is an application note applying to S2R72A54 of the Hub controller LSIs supporting USB 2.0.

This document describes the mode settings, system configuration, circuit examples, and PCB design precautions. For hardware information on this LSI, refer to the data sheet.

## 2. Power Mode Description

---

## 2. Power Mode Description

This LSI includes PMODE pin, enabling the power mode to be set to suit the hub system configuration.

### 2.1 VBUS power supply mode settings

The VBUS power supplied to the downstream port can be switched on and off using a VBUS switching IC or similar. This enables the system to be protected by switching off the VBUS supply when an overcurrent exceeding the stipulated rating is detected in the downstream. This function can be achieved by connecting the VBUS switching IC to the Dn\_VBUSEN and Dn\_VBUSFLG pins on this LSI. The following control modes can be selected for this LSI.

Table 2.1 PMODE settings

PMODE	VBUS supply mode
H	Individual mode
L	Gang mode

Note that the individual pin logic is as shown below in either Individual or Gang modes.

Table 2.2 VBUSEN and VBUSFLG pins logic

pins	logic
Dn_VBUSEN	Positive logic (VBUS output on for H)
Dn_VBUSFLG	Negative logic (Overcurrent detection for L)

If the Dn\_VBUSFLG pin receives a Low input, it will be treated as overcurrent detection by the LSI, and the Dn\_VBUSEN pin operates to give a Low output within 6 ms to stop the VBUS supply. At the same time, those downstream port's VBUS status change causes the HUB\_OVER\_CURRENT status bit of the Hub Status (when Gang mode) or PORT\_OVER\_CURRENT status bit of the Port Status (when Individual mode) on. Those statuses are reported on replies for GetHubStatus() request or GetPortStatus() request. Notification of those changes in the status is given to the USB host via the interrupt pipe on the hub.

### Individual mode

This mode allows overcurrent detection and VBUS supply on/off switching for each individual downstream port. VBUS switching ICs are required corresponding to the number of ports, but overcurrent detected in one port does not affect the VBUS supply to other ports.

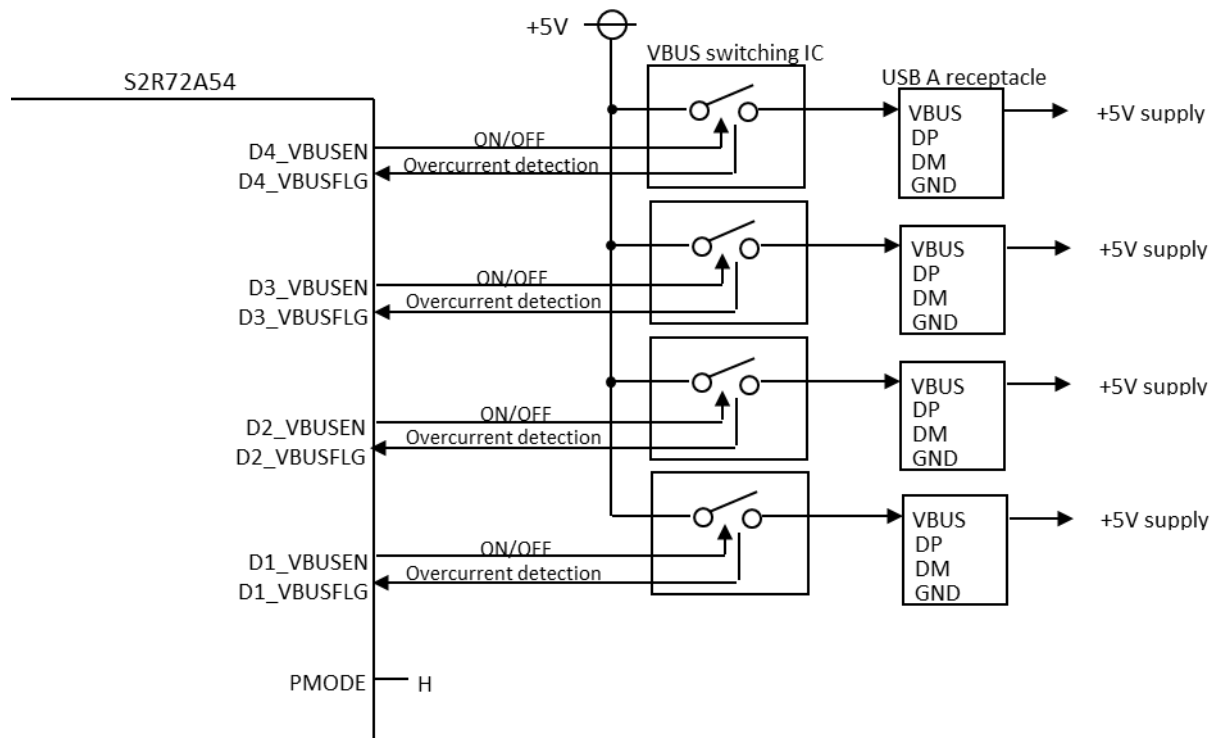


Figure 2.1 Individual mode

## 2. Power Mode Description

### Gang mode

This mode achieves combined overcurrent detection and VBUS supply on/off switching of all downstream ports by using port1 pins(D1\_VBUSEN and D1\_VBUSFLG pins). This requires only one switching unit, but means that overcurrent detection affects the VBUS supply to all ports.

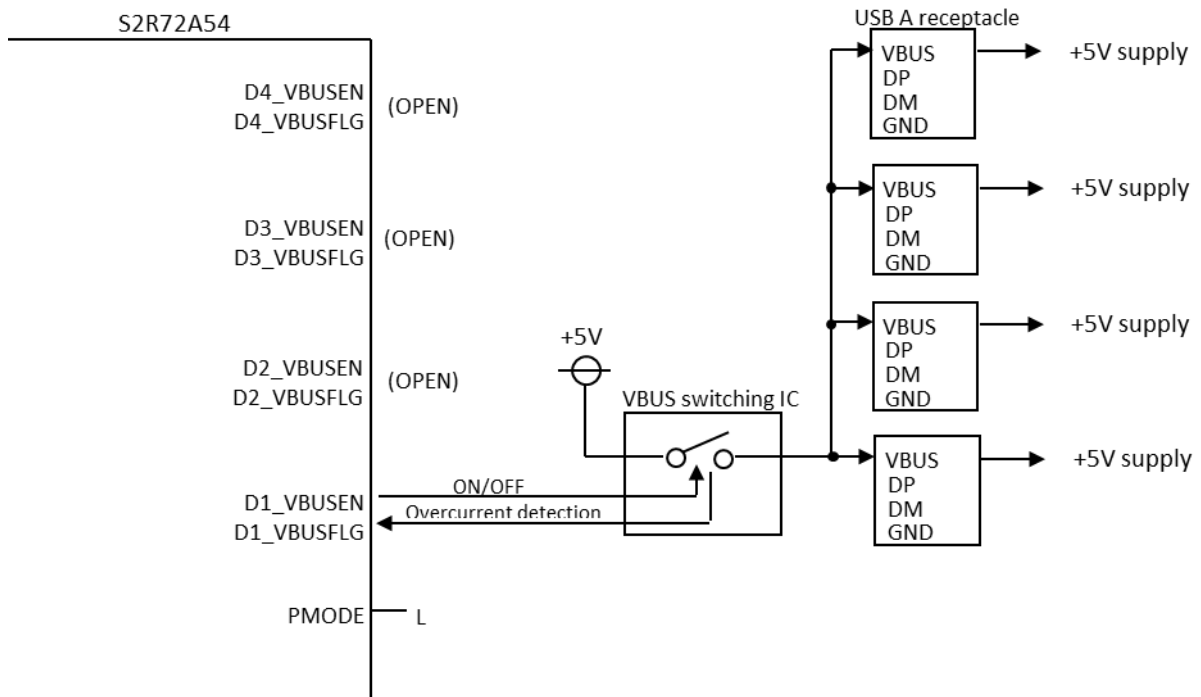


Figure 2.2 Gang mode

### Non-control mode

In this mode, the LSI is not involved with VBUS supply. In other words, overcurrent detection status of the VBUS supply to downstream cannot be reported to the USB host. From a safety viewpoint, a protective device of some sort should ideally be included at an appropriate position. Note that the Dn\_VBUSEN and Dn\_VBUSFLG pins should be left open in this mode.

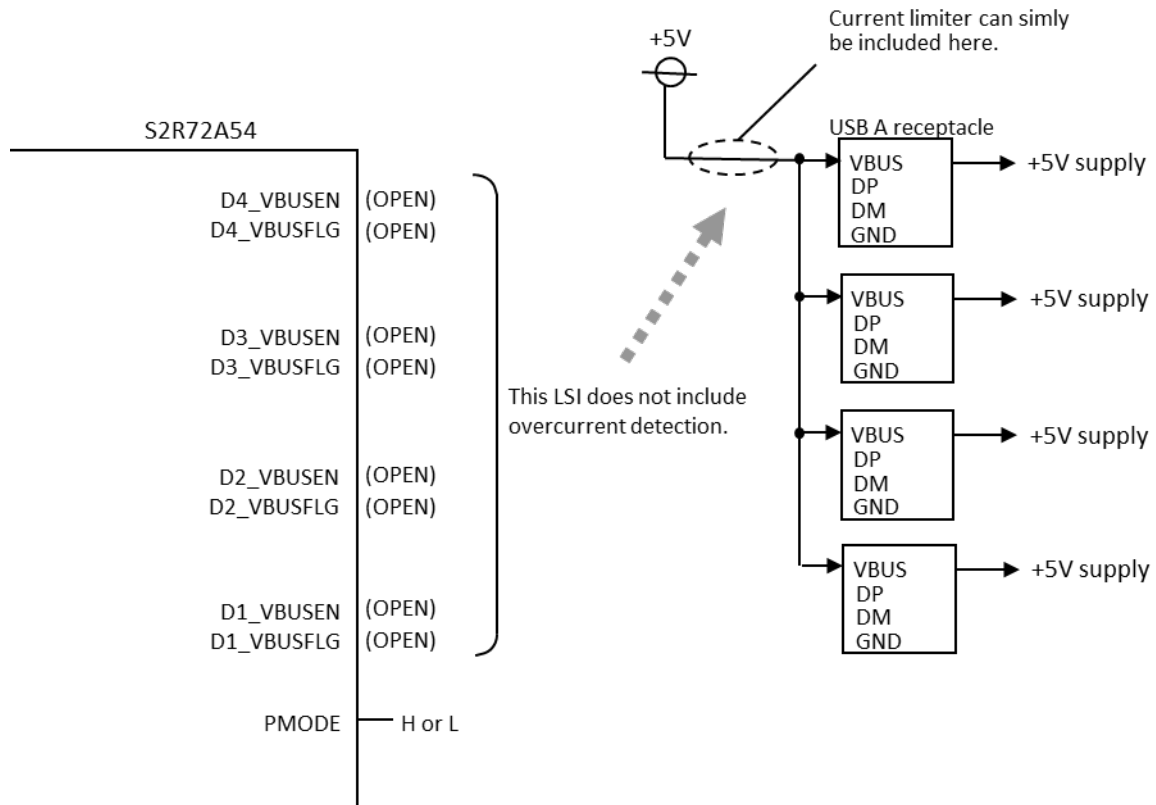


Figure 2.3 Non-control mode



## 2. Power Mode Description

---

### 2.2 Treatment of downstream port not used

This LSI is enabled all four downstream ports. This LSI does not have a selection whether to use the downstream ports. When there are downstream ports not used, these ports should treat as following table.

Table 2.3 Treatment of downstream port not used

pins	Treatment of pins not used
Dn_DP	Open
Dn_DM	Open
Dn_VBUSEN	Open
Dn_VBUSFLG	Open

### 3. PCB Design Guide

#### 3.1 Power supply configuration

There are two main hub device power supply configurations, as shown below, but this LSI does not support the bus-powered configuration. The self-powered configuration should be considered for use.

##### Self-powered configuration

In this configuration, the hub device operates equipped with its own local power supply. The power supply to each downstream port is required to have a capacity of up to 500 mA for each port.

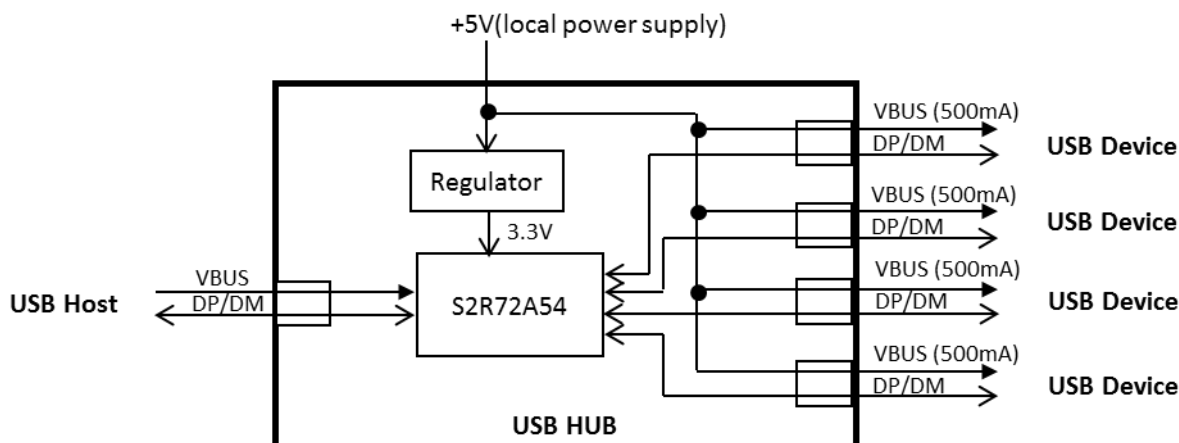


Figure 3.1 Self-powered configuration

##### Bus-powered configuration (not supported)

In this configuration, the hub device operates using the VBUS power supply from the upstream port. The power supply to each downstream port is required to have a capacity of up to 100 mA for each port. However, this LSI does not support this power supply configuration, as the bmAttributes value in the Configuration descriptor returned to the host by the LSI is "SelfPowered" and also the bMaxPower value is 0x32 (max 100 mA).

 


Figure 3.2 Bus-powered configuration (not supported)

### 3. PCB Design Guide

---

#### 3.2 Power supply and resetting

This section describes the power supplied to the LSI.

##### Power supply on/off sequence

The power supplied to this LSI consists of an HVDD power supply (3.3 V) , and an 1.8V power for internal circuit is supplied from internal regulator. Therefore this LSI is not need the on/off sequence and timing specifications.

Note that connecting the USB host to the upstream port while the LSI is not supplied a power does not affect the LSI.

##### Noise

Noise on the power supply may affect the USB waveform quality and cause USB communication problems. Care must be taken when designing the power supply to avoid external noise or ripple noise due to irregular series regulator oscillation or if the switching regulator circuit constants are inappropriate.

##### Resetting

Once the power supply to the LSI has been turned on, perform reset cancellation by setting the XRESET pin from Low to High. Note that oscillation starts once reset cancellation has been performed and the U0\_VBUS pin is subjected to a High level voltage. It is therefore not necessary to perform reset cancellation sequences after oscillation stabilization.

Power supply design

Peak current which appears momentary while there is bus traffic should be considered in power supply design. For example, current consumption on HVDD increases approximately 18mA per hub's transmitting port as compared with the bus is in the idle state, when this LSI is working on the HS mode. It is because of the LSI's power save feature which saves HS transmitter current while it is not transmitting. Power source capacity must cover those current increases.

Below example is showing a current wave form captured with Seiko Epson S5U2R72A54F0100 evaluation board and how it is taken.

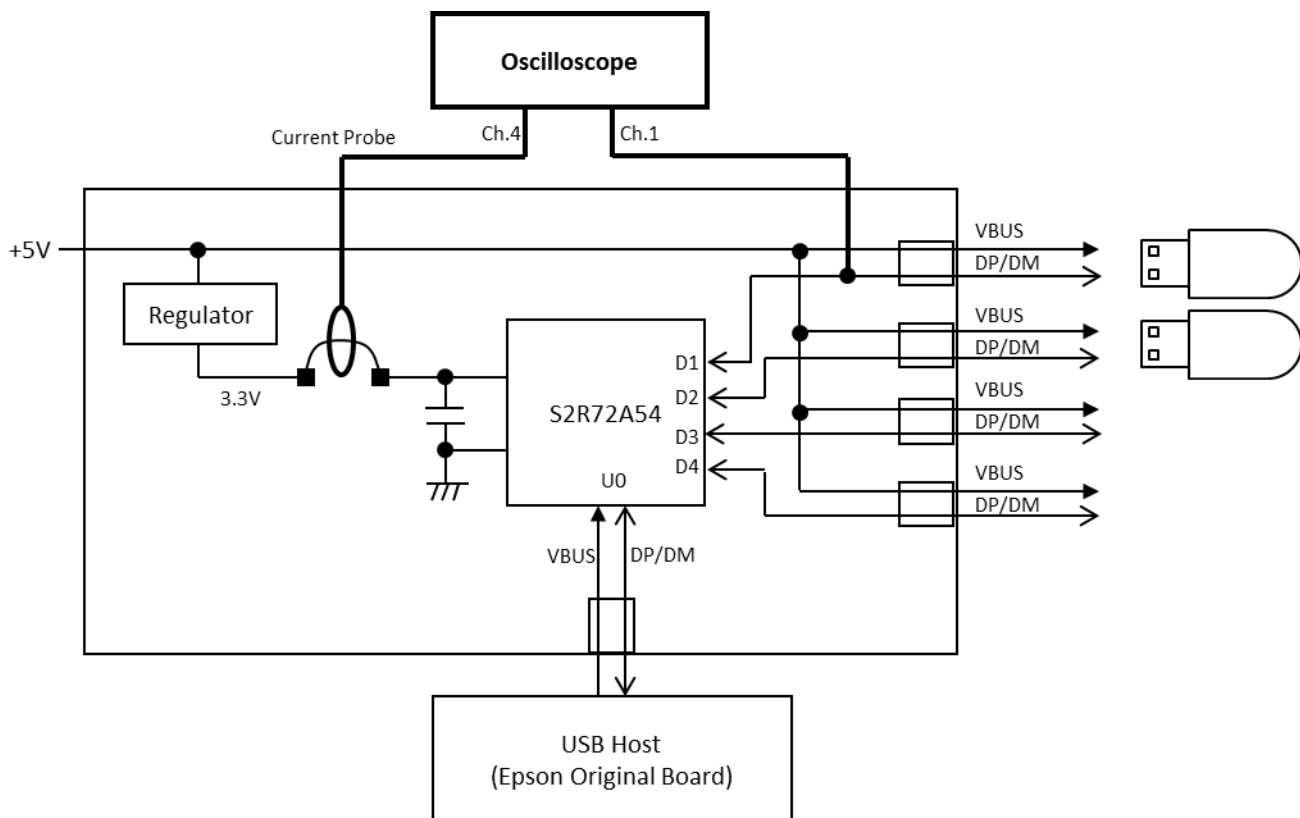


Figure 3.3 Measurement environment

### 3. PCB Design Guide

---

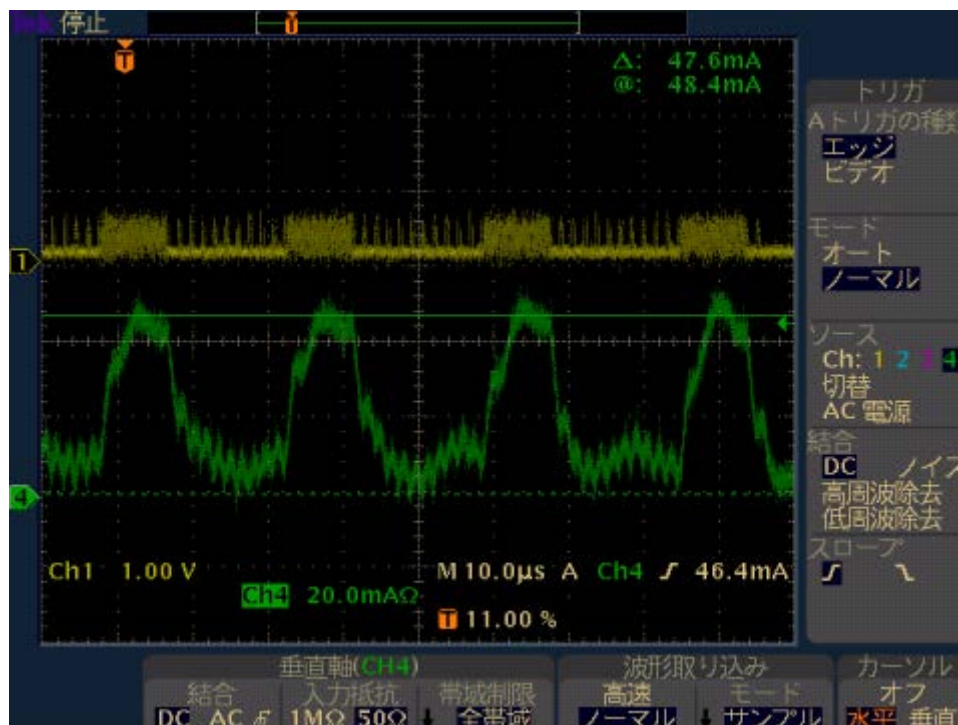


Figure 3.4 Current wave form example

- Ch1(yellow line) : DP line on the bus
- Ch4(green line) : Current on HVDD

Note that such measured values depend on power source conditions such as regulator characteristics, power line impedance, circuit structure, temperature etc.

### 3.3 DP/DM signal line

#### 3.3.1 Circuit board wiring

The following points should be taken into consideration for the DP/DM signal wiring to ensure impedance matching and prevent reflection. Refer to the practical examples given in the Appendix.

- The differential impedance in the DP/DM signal line must be  $90\ \Omega$ .
- Sufficient attention must be paid to impedance matching if other connectors and cables are inserted between the LSI and the USB receptacle.
- The lining layer directly below the signal line must be a non-separated GND plane.
- Signal lines that are considered noise sources (e.g. clock, high-speed bus line) must be kept away from the DP/DM line.
- A pair of DP/DM signal lines should be parallel and of equal length, and should be kept as short as possible. Branches should be minimized, and curved lines should be subject to curved wire treatment.

Note that USB standards stipulate respective transmission delay times for signals within devices, and the following conditions must be satisfied. The signal line lengths to comply with these stipulations will vary depending on parameters such as the dielectric constant,  $\epsilon_r$ , of the board used.

Between the LSI pins (D1 to D4) and receptacle A pins: Within 3 ns

Between the LSI pin (U0) and receptacle B pins: Within 1 ns

#### 3.3.2 Additional components

##### Common mode choke coil

The common mode choke coil prevents the occurrence of common mode noise by inhibiting current flowing in the same direction in the differential signal line. Use on the DP/DM signal line can be effective in improving skew and in reducing unwanted radiated noise. It is not directly involved in improving Eye-pattern opening. Typical components used for USB High-speed are listed below. Note that components should preferably be installed linearly with respect to the signal line to ensure signal quality.

- TDK           ACM2012-900-2P
- Murata       DLW21SN900SQ2
- Toko          985BH-1007

 


Figure 3.5 Typical common mode choke coil wiring

### 3. PCB Design Guide

---

#### Chip varistor

Use on the DP/DM signal line can be effective in protecting the LSI DP/DM pins from static electricity and surges. Typical components used for USB High-speed are listed below. Note that components should preferably be installed with shortest possible branches from the signal line to ensure signal quality. The chip varistor mounting position is generally considered more effective in the vicinity of the connectors, but this should be determined after consulting with the respective manufacturers.

- TDK AVR Series
- Panasonic Electronic Devices EZJZ Series

 


Figure 3.6 Typical varistor wiring

#### Connector

The DP/DM signal quality may deteriorate if a non-USB certified connector is used. It is recommended that USB-certified connectors be used. The same applies to the cables used.

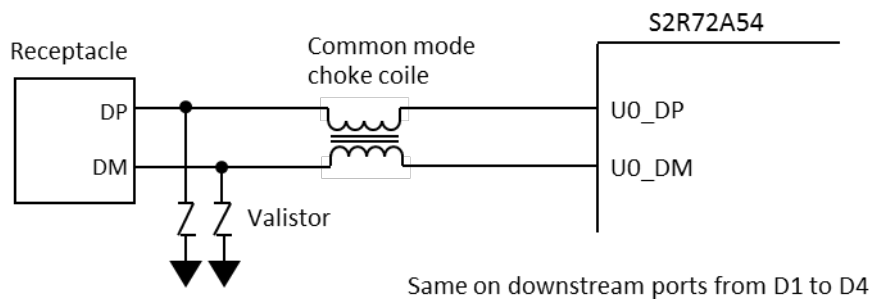


Figure 3.7 DP/DM wiring example

#### Note: Capacity components

Adding parts with capacity components such as chip varistors on the DP/DM signal line will relax the rising and falling ( $T_r/T_f$ ) characteristics of the USB high-speed transmission waveform. Care is necessary when selecting parts, as an excessively large capacity component may cause the  $T_r/T_f$  characteristics or Eye-pattern to fail the USB compliance test.

3.3.3 Terminations

Since this LSI has cable terminations which are defined in the USB2.0 standard on it's silicon inside the pins as shown in figure 3.9, none of those resistors are required to be assembled on PCB.

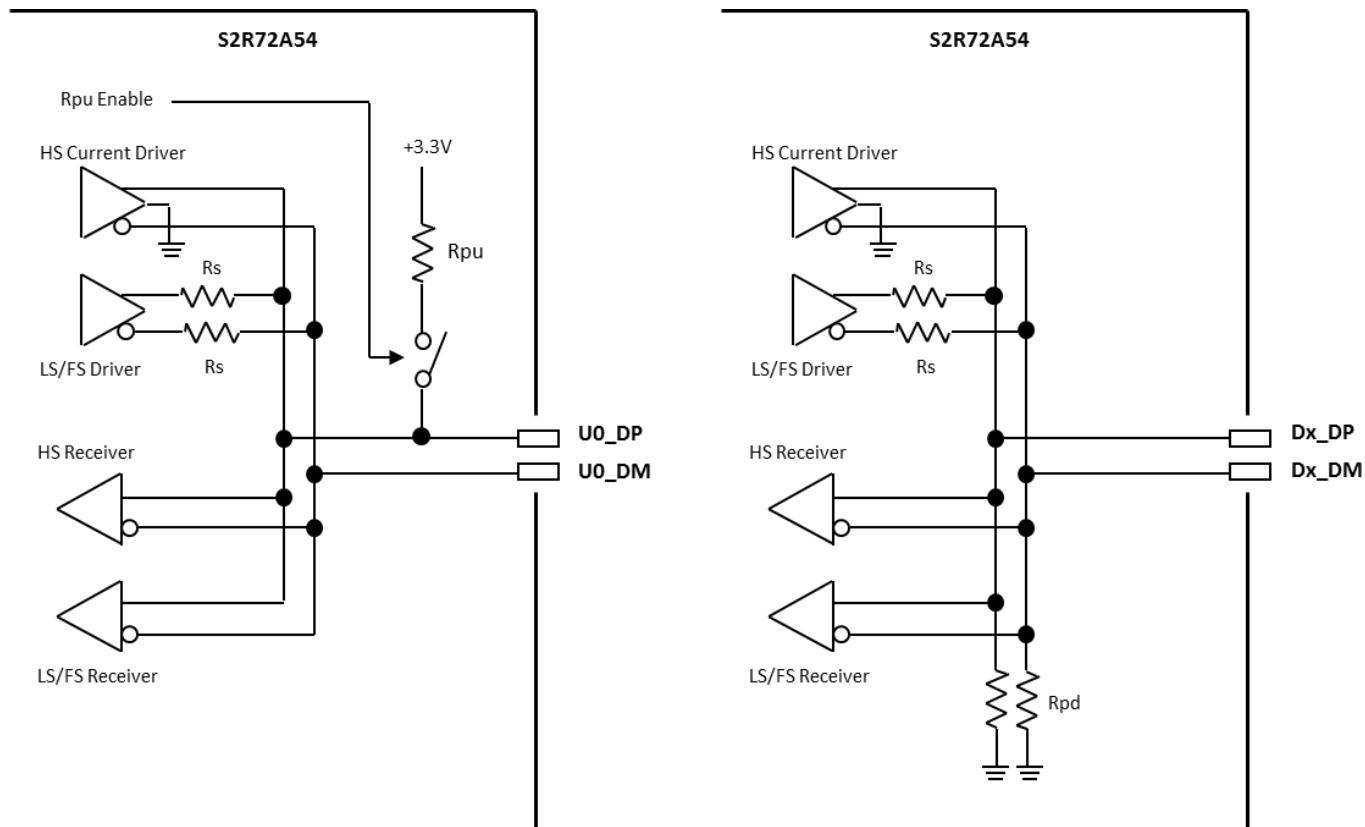


Figure 3.8 Internal termination resistors



### 3. PCB Design Guide

#### 3.4 U0\_VBUS pin protection circuit (upstream port side)

The U0\_VBUS pin may be subjected to a voltage exceeding the VBUS rated voltage (5 V) transiently when connected by the USB cable, depending on the USB host connected to the upstream port. The following protection circuit must be included, as the voltage could exceed the absolute maximum rating of the U0\_VBUS pin and damage the LSI. The protection circuit is not required if there is no concern of voltages exceeding the ratings, such as in the case of internal connections that do not involve cable connection or disconnection. The following points must be noted if the circuit constant is altered, and not only in this case.

- The voltage applied to the U0\_VBUS pin must not exceed the absolute maximum rating (6 V).
- Normally input level of the U0\_VBUS pin is 3.3V, therefore voltage-dividing circuit from 5V to 3.3V must be need in follows figure. And the input level due to the voltage ratio must not be less than the “High” level trigger voltage, refer to the data sheet.
- Refer to “Device Capacitance ECN” from USB.org, VBUS must need to have a capacitance more than 1uF less than 10uF.


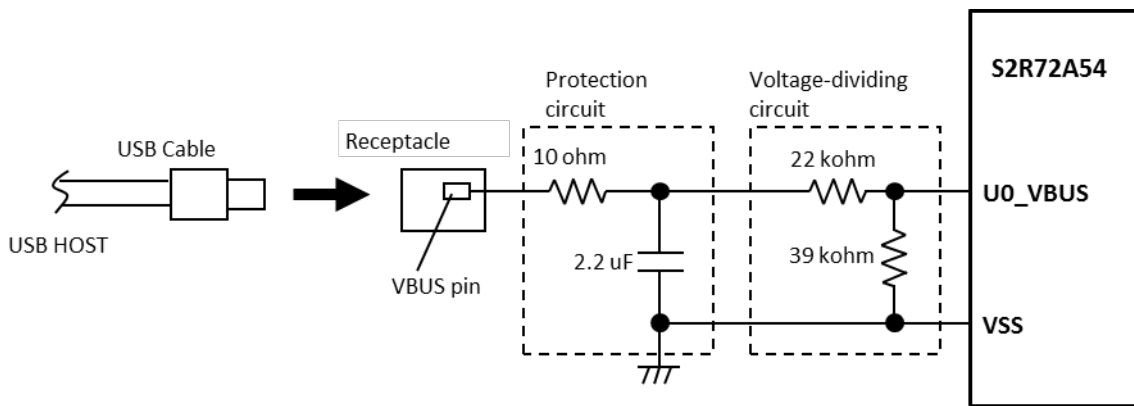


Figure 3.9 U0\_VBUS pin protection circuit

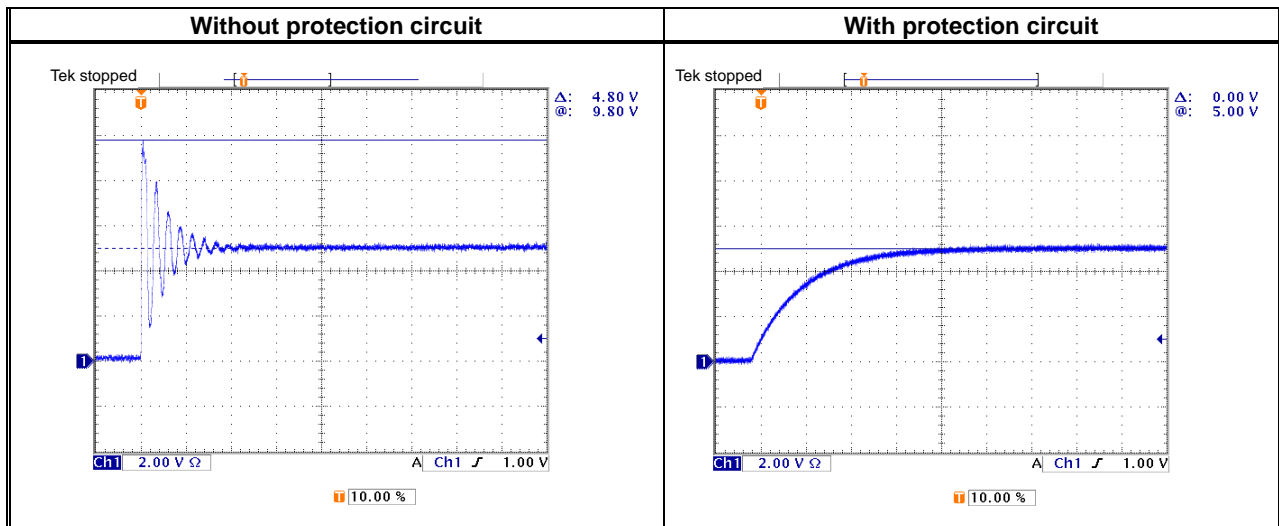

Blue — : VBUS pin voltage


Figure 3.10 U0\_VBUS pin applied voltage leading edge waveform

For hub’s down-ports, there is no notice like that because no device is expected to give electric charge on VBUS.

### 3.5 VBUS supply circuit (downstream port side)

This section describes a typical control circuit to feed the VBUS power supply (+5 V) to the downstream port. The circuit configuration will vary depending on the control mode (Individual/Gang). Here, connection examples are shown for both modes using Maxim MAX8586ETA+ USB power switching ICs with overcurrent detection function.

#### Individual mode

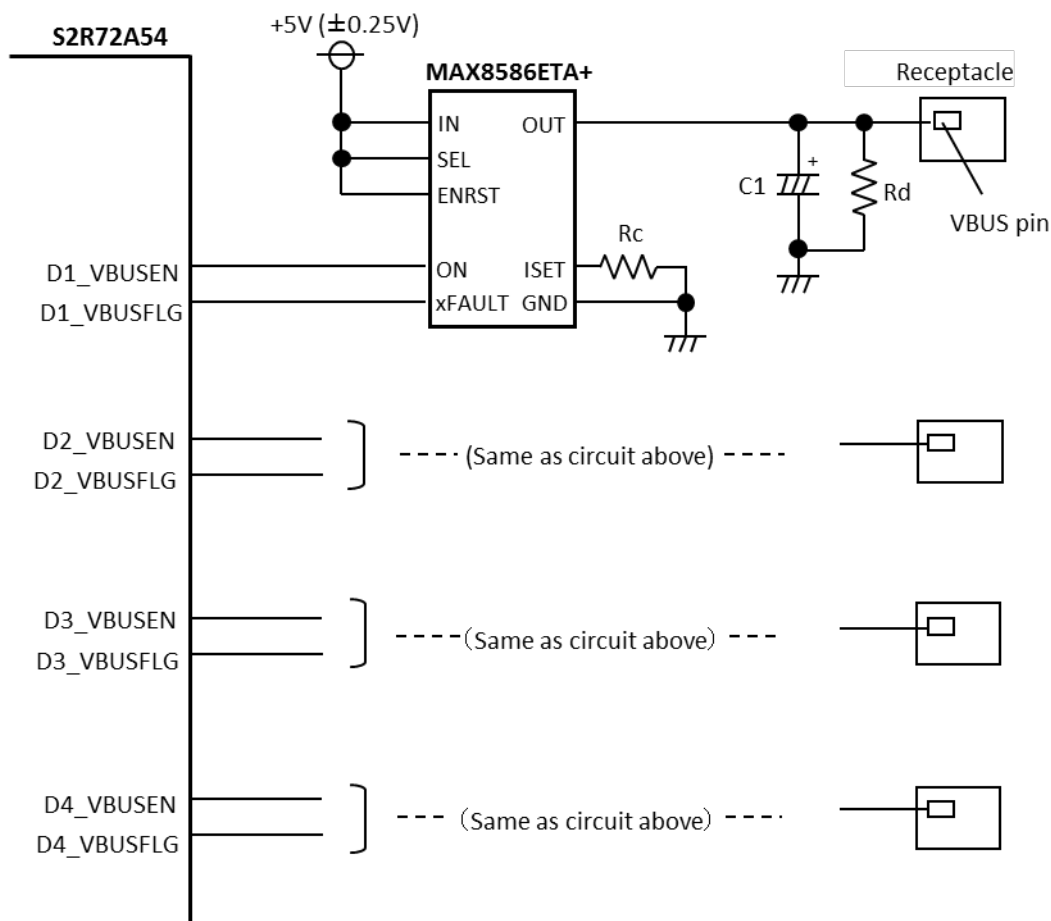

- C1: Stipulated as capacitance of at least 120uF in USB 2.0 standards, section 7.2.4. (220uF for Seiko Epson evaluation board S4U2R72A54F0100)
- R1: Load discharge resistance for when the VBUS switching IC output is shut off with C1 charged and no USB device connected to the receptacle. (100kΩ for Seiko Epson evaluation board S5U2R72A54F0100)
- R2: Resistance for determining the overcurrent detection value. For more information, refer to the MAX8586ETA+ specifications.

Figure 3.11 Individual mode circuit example

### 3. PCB Design Guide

#### Gang mode

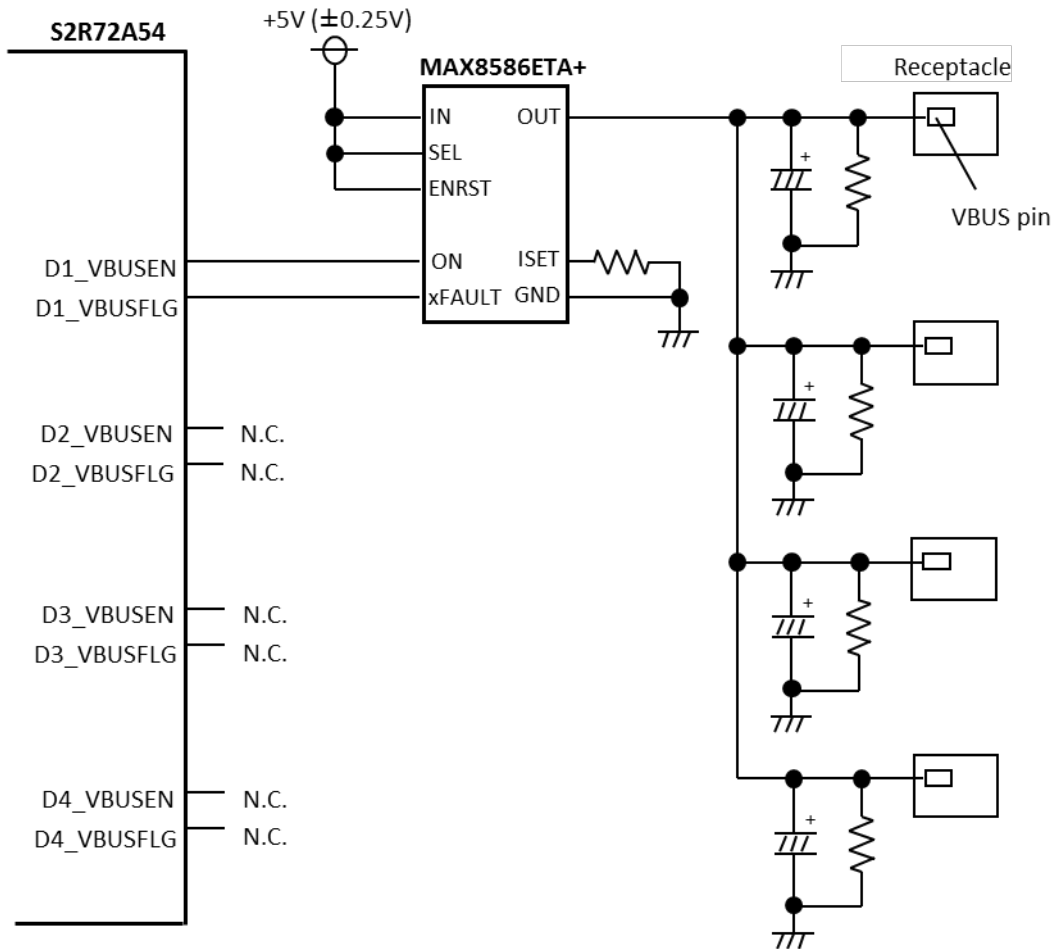


Figure 3.12 Gang mode circuit example

Note: Switch IC consideration

Logic level of VBUS controlling pins of this LSI is fixed as below.

Dn\_VBUSEN pin: Active High (Enables VBUS by High)

Dn\_VBUSFLG pin: Active Low (Indicates over-current by Low)

So, the VBUS switch IC having different specifications should be fitted to it with some external circuit.


 


Figure 3.13 Logic converting circuit example

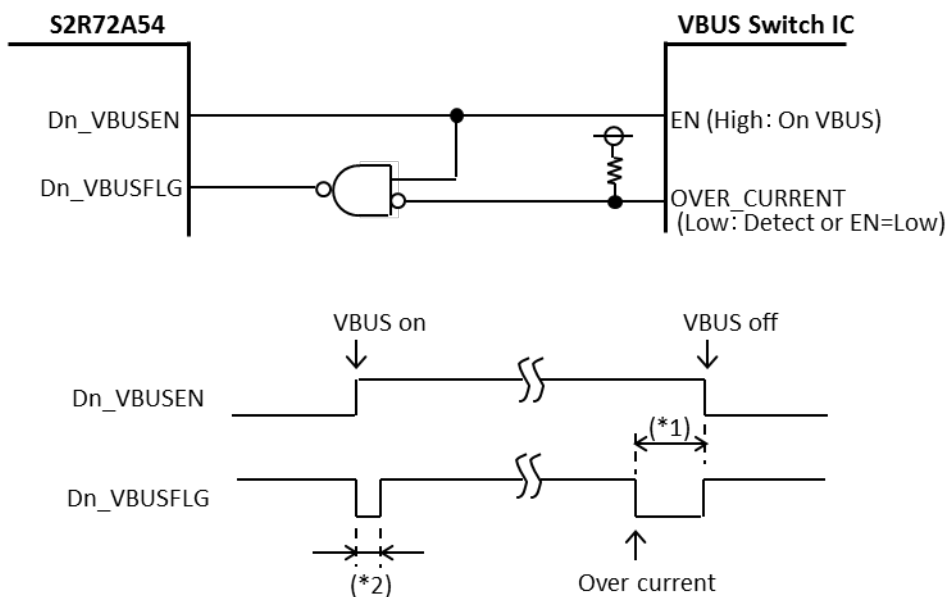It should be also considered that this LSI does not assert Dn\_VBUSEN pin high while Dn\_VBUSFLG pin is kept low. Note that some VBUS switch IC are designed as it asserts over-current detection output while it is disenabled. Combination of this kind of VBUS switch IC and this LSI require a special consideration for external circuit to activate. Below is just an example of such external circuit.



(\*1) S2R72A54 asserts Dn\_VBUSEN low in 6ms after Dn\_VBUSFLG is asserted low.

(\*2) S2R72A54 ignores Dn\_VBUSFLG pulse narrower than 4ms.

Figure 3.14 Adaptor circuit example

### 3. PCB Design Guide

#### 3.6 Oscillator circuit

##### Using a crystal oscillator

A 24 MHz crystal oscillator should be used connected as shown below. The USB high-speed data rate tolerance is  $\pm 500$  ppm, but the crystal oscillator frequency accuracy should preferably be within  $\pm 100$  ppm to ensure satisfactory waveform quality.

Note that oscillation starts once the LSI has been reset cancelled and the U0\_VBUS pin is subjected to a High level voltage. U0\_DP is also pulled up (FS termination) when PLL is locked after oscillation stabilized.

 


Figure 3.15 Typical crystal oscillator connection circuit

Recommended device (for vehicle mounting): Seiko Epson FA-238A ( $C_L = 7$  pF) PN#: X1E000341014900

Typical constants for Seiko Epson evaluation board:  $C_g = 6$  pF,  $C_d = 7$  pF,  $R_d = 0 \Omega$

##### Using a clock signal

When inputting an external clock signal without using a crystal oscillator, it should be input to the XI pin when power is provided to the LSI. The XO pin should be left open. The clock input can be provided to the XI pin when the U0\_VBUS pin input status is either H or L. The clock signal duty ratio is 45% to 55%, and the amplitude is the same as for the LVDD voltage level. The tolerances are the same as for the crystal oscillator.

 


Figure 3.16 External clock input

### 3.7 Other precautions

#### Resistance connected to R1 pin

A  $6.04\text{ k}\Omega \pm 1\%$  resistance should be positioned as close as possible to the R1 pin. This is used to generate the standard reference current which determines the USB analog circuit characteristics, so the analog characteristics will be affected if the tolerances are overly large. A resistance with the specified accuracy must always be used.

#### FVDD , LVDDC and LVDDM pin

FVDD, LVDDC and LVDDM pins should be need to mounted 0.1uF and 10uF capacitor between VSS. These capacitor should be mounted as close as possible to these pins and in order of 0.1uF and 10uF from pin as follows figure.

 


Figure 3.17 Arrange capacitors about FVDD, LVDDC and LVDDM

#### HVDD pins

Bypass capacitors should be positioned as close as possible to the HVDD pins. The capacitances on Seiko Epson evaluation boards (S5U2R72A54F100) are as shown below, but they will vary depending on the regulator characteristics. It is recommended that they be installed for each power supply pin, to ensure LSI operation stability.

Each HVDD pins:	0.1 $\mu$ F
Supply based of HVDD:	10uF

#### VSS pins

The VSS pins must be connected to a non-separated GND plane (see examples in Appendix) via a low impedance.

## 4. Appendix

## 4. Appendix

### 4.1 DP/DM circuit board wiring examples

Examples are given below showing DP/DM signal wiring between the LSI and the USB receptacle. Note that components added to the DP/DM signal are omitted here. The dimensions are based on manufacturing data for Seiko Epson evaluation boards (manufactured by Sankei).

#### Upstream port side

 


Figure 4.1 B receptacle (through-hole type) example with same-face mounting

#### Downstream port side

 


Figure 4.2 A receptacle (through-hole type) example with same-face mounting

## 4.2 Upstream port connection example

The sequence from HS connection to the upstream port until the downstream port is enabled is described below using the diagram below as an example.

 


Figure 4.3 Oscillation waveform example

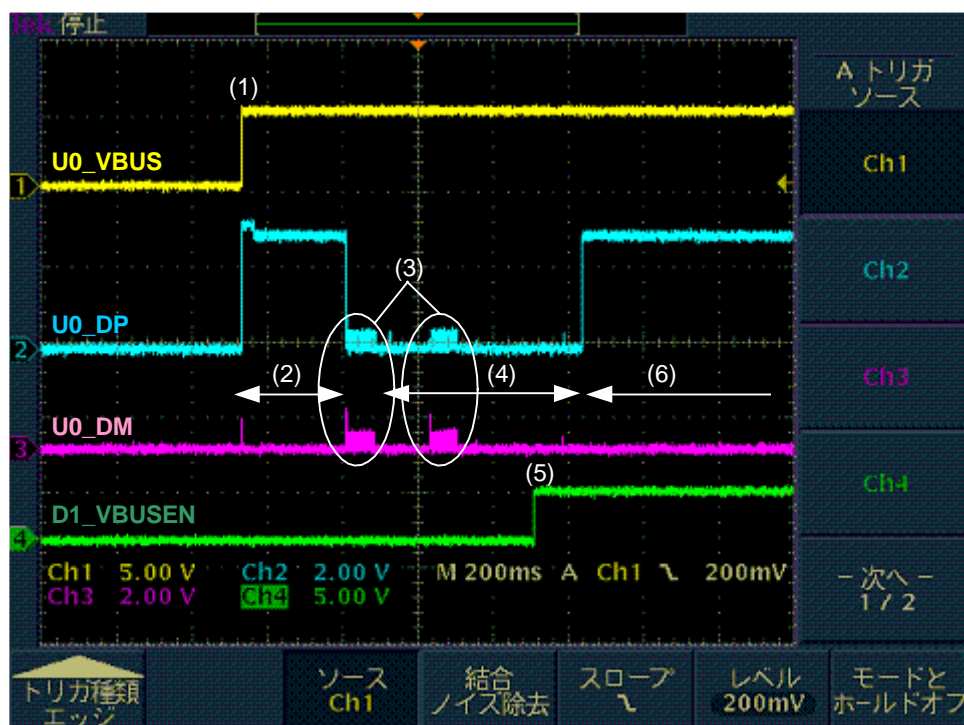


Figure 4.4 Upstream port connection example



## 4. Appendix

---

(1) U0\_VBUS High detection and OSC oscillation

Connecting to a USB host via a cable causes the U0\_VBUS pin to switch to High. This triggers the LSI to start internal oscillation.

(2) DP pull-up

After PLL is locked following stabled oscillation and detected the U0\_VBUS pin High level, the LSI pulls up the U0\_DP pin using the internal resistance.

(3) Bus resetting and chirping

The LSI returns a Chirp K on receiving a bus reset from the USB host shortly after the U0\_DP pin is pulled up. A host chirp is issued from the host in response to this. The speed negotiation is thus completed as High Speed.

(4) Enumeration

The LSI responds to the various requests issued from the host. (The packet waveform is not shown sufficiently in the diagram above.)

(5) Downstream port VBUS enabling

The Dn\_VBUSEN pin switched to High in step (4) described above. (x = 1 to 4) This is performed on receiving a SetPortFeature (PORT\_POWER) request from the host. The VBUS supply to the downstream port is started using this signal.

(6) Suspended state

In this example, the U0 port enters suspended state once the processing in (4) and (5) above ends. This is because no USB device is connected to the downstream port and no packet is transmitted in this example, and so the upstream port enters suspended state. If a USB device is connected, connection processing with the device starts and the U0 port does not enter suspended state.

### 4.3 Downstream port overcurrent detection example

The diagram below shows the sequence from detection of an overcurrent in the VBUS power supplied to the downstream port until the VBUS supply stops. The example below is for Individual mode. The requests used will differ in Gang mode, but the sequence is the same.

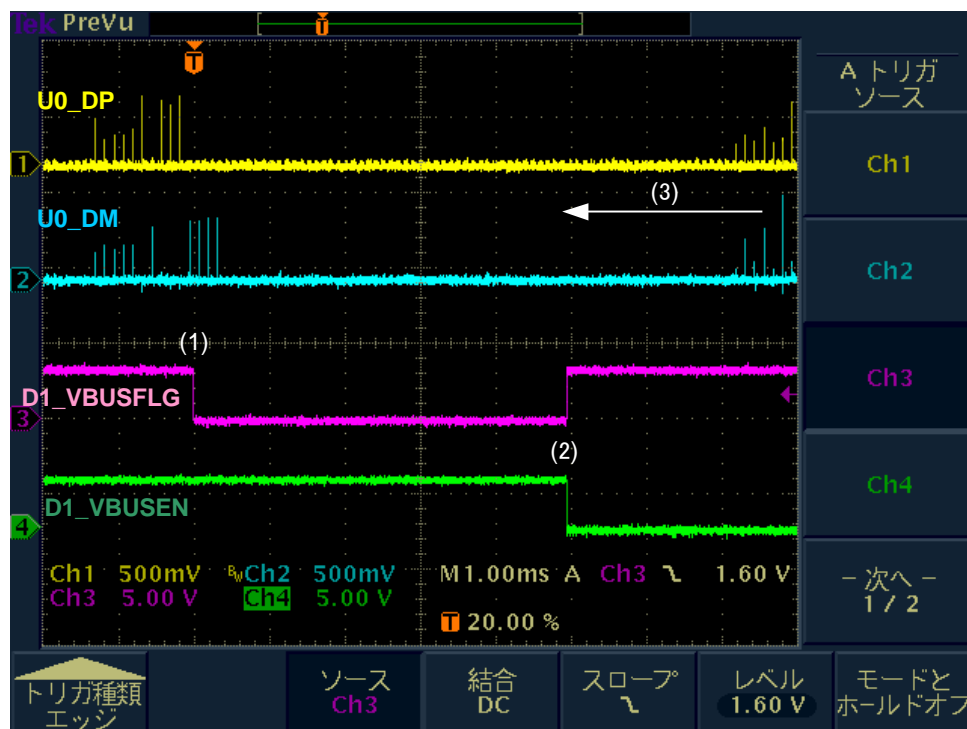


Figure 5.5 Overcurrent detection example

(1) Overcurrent detection

Overcurrent occurrence is detected when a Low level signal is input to the D1\_VBUSFLG pin from the external VBUS switching IC, etc. The condition corresponding to overcurrent depends on the VBUS switching IC's specifications and settings.

(2) Downstream port VBUS disabling

The D1\_VBUSEN pin outputs a Low signal within 6 ms after (1) above. The VBUS supply to the downstream port is stopped using this signal. In this example, the signal input to the D1\_VBUSFLG pin returns to High level at the same time. This is because the external VBUS switching IC no longer detects overcurrent.

(3) Status change notification and request response

The host detects that the overcurrent status has changed in the VBUS port of the LSI's downstream side using the following sequence.

## 4. Appendix

---

1. The host detects that StatusChange bit has been set for the port in which the overcurrent field changed using Interrupt-IN transfer.
2. The host issues a GetStatus request, and the LSI notifies by setting the PortChangeBits C\_PORT\_OVER\_CURRENT bit. (Note 1)
3. The host issues a ClearFeature (C\_PORT\_OVER\_CURRENT) request.

Note 1: The PortStatusBits PORT\_OVER\_CURRENT bit is not normally set, as the VBUS supply is stopped and the overcurrent status clears when this request response is issued.

If the host subsequently issues the SetFeature (PORT\_POWER) request, the D1\_VBUSEN pin outputs High, and the VBUS supply is resumed to this downstream port. However, whether or not the SetFeature request is issued depends on the host specifications, as the process described above will be repeated if the fundamental cause of the overcurrent occurrence remains unchanged.

### 4.4 Device malfunction detection and recovery

Though a hub is not expected to detect device's malfunction because it has no mechanism to do that other than detach and over-current, it still has an ability to recover a system from devices' temporary failure conditions. For example, followings are possible recovering procedures which hub can serve.

1. VBUS negation

Off the VBUS by ClearPortFeature(PORT\_POWER) request to hub's corresponding port.

On the VBUS again by SetPortFeature(PORT\_POWER) request.

2. Bus reset

Force hub's down-port bus reset by SetPortFeature(PORT\_RESET) request to hub's corresponding port.

Note that bus reset is not an almighty method to recover a device while hard reset is, because it is a kind of bus protocol handled by a device's usb controller which might be malfunction.

## Revision History

---

### Revision History

Date	Revision details			
	Rev. No.	Page	Category	Details
Apr. 1, 2016	0.80	All	New	Newly established
Jul. 1, 2016	0.90	P.6	Revice	Changed from "Stable high" to "Open" when Dn_VBUSFLG not used.
		P.14	Add	Capacitance of VBUS need more than 1uF less than 10uF
			Revice	In Figure 3.9, Capacitance of VBUS is changed from "1uF" to "2.2uF".
Jul. 12, 2016	0.91	P.5	Revice	In Figure 2.3, changed from "H" to "(OPEN)" when Dn_VBUSFLG not used.
Oct. 28, 2016	1.00	All	Established	Established with qualified mass production
		-	Revice	Revised Section 5.3 to 4.3, and Section 5.4 to 4.4.
Apr. 6, 2017	1.01	P.19	Revice	Changed R1 resistor value from "6.2 kΩ" to "6.04 kΩ".
June. 22, 2017	1.02	P.18	Revice	Add to Recommended device "PN#: X1E000341014900"

### AMERICA

---

**EPSON ELECTRONICS AMERICA, INC.**

214 Devcon Drive,  
San Jose, CA 95112, USA  
Phone: +1-800-228-3964      FAX: +1-408-922-0238

### EUROPE

---

**EPSON EUROPE ELECTRONICS GmbH**

Riesstrasse 15, 80992 Munich,  
GERMANY  
Phone: +49-89-14005-0      FAX: +49-89-14005-110

### ASIA

---

**EPSON (CHINA) CO., LTD.**

4th Floor, Tower 1 of China Central Place, 81 Jianguo Road, Chaoyang  
District, Beijing 100025 China  
Phone: +86-10-8522-1199      FAX: +86-10-8522-1120

**SHANGHAI BRANCH**

Room 1701 & 1704, 17 Floor, Greenland Center II,  
562 Dong An Road, Xu Hui District, Shanghai, CHINA  
Phone: +86-21-5330-4888      FAX: +86-21-5423-4677

**SHENZHEN BRANCH**

Room 804-805, 8 Floor, Tower 2, Ali Center, No.3331  
Keyuan South RD (Shenzhen bay), Nanshan District, Shenzhen  
518054, CHINA  
Phone: +86-10-3299-0588      FAX: +86-10-3299-0560

**EPSON TAIWAN TECHNOLOGY & TRADING LTD.**

14F, No. 7, Song Ren Road,  
Taipei 110, TAIWAN  
Phone: +886-2-8786-6688      FAX: +886-2-8786-6660

**EPSON SINGAPORE PTE., LTD.**

1 HarbourFront Place,  
#03-02 HarbourFront Tower One, Singapore 098633  
Phone: +65-6586-5500      FAX: +65-6271-3182

**SEIKO EPSON CORP.****KOREA OFFICE**

19F, KLI 63 Bldg., 60 Yoido-dong,  
Youngdeungpo-Ku, Seoul 150-763, KOREA  
Phone: +82-2-784-6027      FAX: +82-2-767-3677

---

**SEIKO EPSON CORP.****SALES & MARKETING DIVISION****Device Sales & Marketing Department**

421-8, Hino, Hino-shi, Tokyo 191-8501, JAPAN  
Phone: +81-42-587-5816      FAX: +81-42-587-5116